

CPU Architecture

LAB3 assignment

**Digital System Design with VHDL
(Multi-cycle CPU design)**

Hanan Ribo

09/06/2024

Table of contents

1.	Aim of the Task:	3
2.	Assignment definition:	3
3.	Controller based system:	3
4.	File based simulation of DUT:	7
5.	Running Code Example:.....	8
6.	Requirements:	9
7.	Grading Policy	10

1. Aim of the Task:

- System design using concurrent and sequential logic principles using advanced Simulation methods (based on material given in LAB1 and LAB2 tasks).
- Controller design based on methodology of Control and Datapath separation.
- Preparation for LAB4 task – FPGA based design synthesis of a given design.
- Proper analysis and understanding of architecture design.
- Performing and understanding functional validation and verification of an architecture design.

2. Assignment definition:

In this task, you are required to design a controller-based processing machine as a Multi-cycle CPU in order to run a given program code. The preparation material for this lab has been learned in the prerequisites course “Central Processing Unit Architecture - theory” until lecture five and includes in addition to the self-learning material given on a subjects of FSM methodology design and advanced functional verification.

3. Controller based system:

 


Figure 1: Overall DUT structure

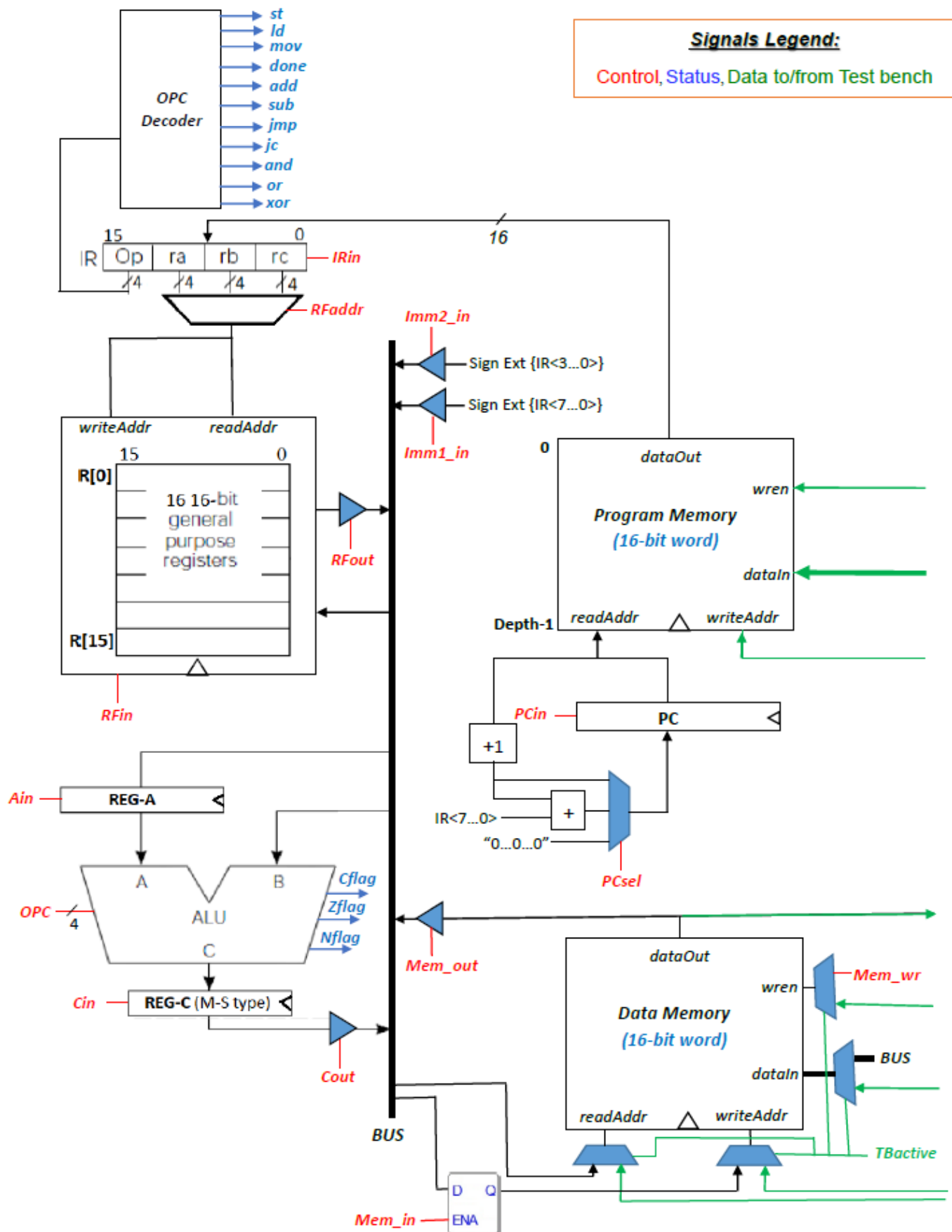


Figure 2: Datapath structure

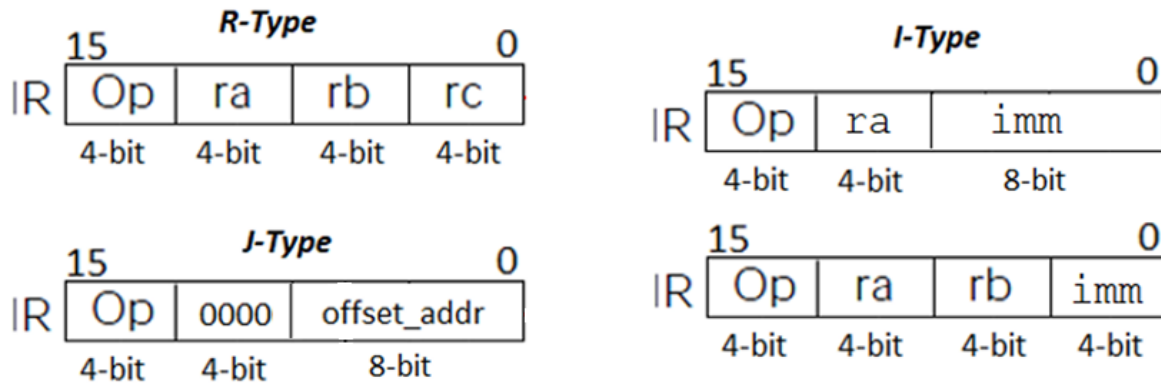


Figure 3: Instruction Formats

Instruction Format	Decimal value	OPC	Instruction	Explanation	N	Z	C
R-Type	0	0000	add ra,rb,rc nop	R[ra]<=R[rb]+R[rc] R[0]<=R[0]+R[0] (<i>emulated instruction</i>)	*	*	*
	1	0001	sub ra,rb,rc	R[ra]<=R[rb]-R[rc]	*	*	*
	2	0010	and ra,rb,rc	R[ra]<=R[rb] and R[rc]	*	*	-
	3	0011	or ra,rb,rc	R[ra]<=R[rb] or R[rc]	*	*	-
	4	0100	xor ra,rb,rc	R[ra]<=R[rb] xor R[rc]	*	*	-
	5	0101	<i>unused</i>				
	6	0110	<i>unused</i>				
J-Type	7	0111	jmp offset_addr	PC<=PC+1+offset_addr	-	-	-
	8	1000	jc /jhs offset_addr	If(Cflag==1) PC<=PC+1+offset_addr	-	-	-
	9	1001	jnc /jlo offset_addr	If(Cflag==0) PC<=PC+1+offset_addr	-	-	-
	10	1010	<i>unused</i>				
	11	1011	<i>unused</i>				
I-Type	12	1100	mov ra,imm	R[ra]<=imm	-	-	-
	13	1101	ld ra,imm(rb)	R[ra] <= M[imm+R[rb]]	-	-	-
	14	1110	st ra,imm(rb)	M[imm+R[rb]] <= R[ra]	-	-	-
	15	1111	done	Signals the TB to read the DTCM content	-	-	-

Note: * The status flag bit is affected , - The status flag bit is not affected

Table 1 : Multi-cycle CPU ISA

Control Unit

Signals Legend: Control, Status, Data to/from Test bench

 


Figure 4: Control unit structure

 


Figure 5: Single Port RAM with an unregistered output (this structure used for Register File and Program Memory with a given VHDL code)


 


Figure 6: Single Port RAM with a registered output (this structure used for Data Memory with a given VHDL code)

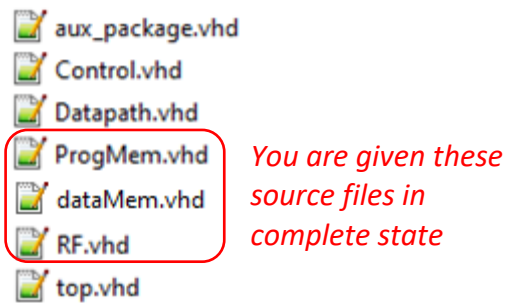
- The given files that you must use in your project:



- ✓ You must use the listed above source files, you are required to fill them up yourself.
- ✓ You can add additional VHDL source code files.
- ✓ Other entities can be designed and modeled behaviorally, structurally, etc.

 4. File based simulation of DUT:

- As depicted in figure 1, in order to simulate the system DUT we use file based simulation.
- Two Input and one Output files structure (according the above given figure at clause 3):



5. Running Code Example:

```

1  data segment:
2  arr dcl6 20,11,2,23,14,35,6,7,48,39,10,11,12,13
3  res ds16 1
4
5  code segment:
6  ld r1,4(r0)
7  ld r2,5(r0)
8  mov r3,31
9  mov r4,1
10 mov r5,14
11 and r1,r1,r3
12 and r2,r2,r3
13 sub r6,r2,r1
14 jc 2
15 add r6,r4,r0
16 jmp 1
17 add r6,r0,r0
18 st r6,0(r5)
19 done
20 nop
21 jmp -2

```

*Assembly
code*

```

1  int arr[14]={20,11,2,23,14,35,6,7,48,39,10,11,12,13}
2  int res;
3
4  void main() {
5
6      R[1] = arr[4] & 31;
7      R[2] = arr[5] & 31;
8
9      if(R[2] >= R[1])
10         res=0;
11     else
12         res=1;
13
14     loop_forever;
15
16 }

```

*Equivalent
Pseudo
code*

ITCMinit.txt	DTCMinit.txt	DTCMcontent.txt
1 D104	1 0014	1 0014
2 D205	2 000B	2 000B
3 C31F	3 0002	3 0002
4 C401	4 0017	4 0017
5 C50E	5 000E	5 000E
6 2113	6 0023	6 0023
7 2223	7 0006	7 0006
8 1621	8 0007	8 0007
9 8002	9 0030	9 0030
10 0640	10 0027	10 0027
11 7001	11 000A	11 000A
12 0600	12 000B	12 000B
13 E650	13 000C	13 000C
14 F000	14 000D	14 000D
15 0000	15 0000	15 0001
16 70FE		

*Updated
values
after
program
run*

6. Requirements:

1. The design must be well commented.
2. Elaborated analysis and wave forms:
 - Remove irrelevant signals.
 - Zoom on regions of interest.
 - Draw clouds on the waveform with explanations of what is happening (Figure 4).
 - Change the waveform colors in ModelSim for clear documentation
(Tools->Edit Preferences->Wave Windows).
3. A ZIP file in the form of **id1_id2.zip** (where id1 and id2 are the identification number of the submitters, and id1 < id2) *must be upload to Moodle only by student with id1* (any of these rules violation disqualifies the task submission).
4. The **ZIP** file will contain (*only the exact next sub folders*):

Directory	Contains	Comments
DUT	Project VHDL files	Only VHDL files of DUT , excluding test bench Note: your project files must be well compiled without errors as a basic condition before submission
TB	VHDL files that are used for test bench	One tb.vhd for the Datapath One tb.vhd for the Control unit One tb.vhd for the overall DUT
SIM	ModelSim DO files (wave, list)	One tb.vhd for the Datapath One tb.vhd for the Control unit One tb.vhd for the overall DUT (with Datapath and Control unit signals included)
DOC	Project documentation	<ul style="list-style-type: none">• readme.txt (list of the DUT *.vhd files with their brief functional description)• pre3.pdf (report file that includes brief explanation of the top module with its wave diagrams as shown in figure 4)• designGraph.pdf (elaborated FSM graph of your DUT)

Table 2: Directory Structure

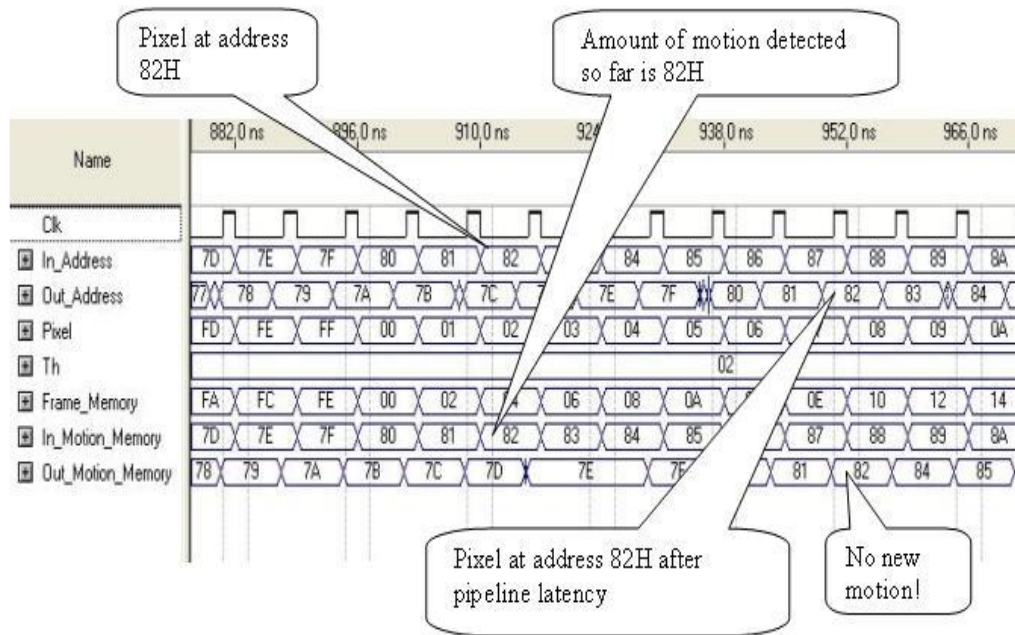


Figure 4: Clouds over the waveform example

7. Grading Policy

Weight	Task	Description
10%	Documentation	The "clear" way in which you presented the requirements and the analysis and conclusions on the work you've done
90%	Analysis and Test	The correct analysis of the system (under the LAB3 SEAT requirements)

Table 3: Grading

Under the above policies you'll be also evaluated using common sense:

- Your files will be compiled and checked, the system must work.
- Your design and architecture must be intelligent, minimal, effective and well organized.